

Problem 2

I. Answer the following questions regarding transmission line circuits. Voltage and current are expressed by complex notation, the angular frequency is ω , and the imaginary unit is j . The circuits are in a stationary state.

(1) Fig. 1 shows the equivalent circuit of a lossless transmission line with an inductance per unit length of L and a capacitance per unit length of C .

(1-i) Find the complex impedances of the inductor and the capacitor in the small area enclosed by the dotted line between the position x and $x + dx$.

(1-ii) The current and the voltage at the position x are I and V , respectively. The current and the voltage at the position $x + dx$ are $I + dI$ and $V + dV$, respectively. Write down two first-order differential equations with respect to x , which hold between I and V . The equations should include ω .

(1-iii) Write down the second-order differential equations with respect to x for I and V , respectively.

(1-iv) The general solutions of the second-order differential equations in Question (1-iii) are written as follows:

$$V = Ae^{-\gamma x} + Be^{\gamma x} \quad (i)$$

$$I = \frac{Ae^{-\gamma x}}{Z_0} - \frac{Be^{\gamma x}}{Z_0}, \quad (ii)$$

where A and B are constants. Express γ and Z_0 using ω , L , and C .

(2) The transmission line is terminated by a resistance Z_R at $x = l$ as shown in Fig. 2. The current through and the voltage across the resistor are I_R and V_R , respectively. β is defined as $\omega\sqrt{LC}$.

(2-i) The first term and the second term of both Eq. (i) and Eq. (ii) represent a forward wave and a reflected wave, respectively. Find the relationship between Z_R and Z_0 , when B becomes zero and thus no reflection occurs at $x = l$.

(2-ii) When an input voltage is V_S and an input current is I_S at the input terminal $x = 0$, the complex impedance of the transmission line seen from the input is $Z_S = V_S/I_S$. Express Z_S in the form as shown

below. You may use $\tanh(x) = \frac{e^x - e^{-x}}{e^x + e^{-x}}$.

$$Z_S = Z_0 \frac{\square + \square \tanh(\square)}{\square + \square \tanh(\square)}$$

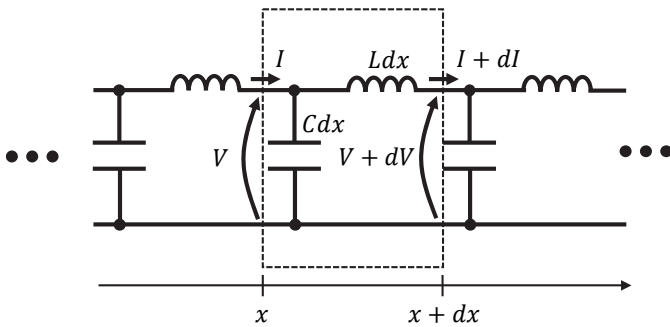


Fig. 1

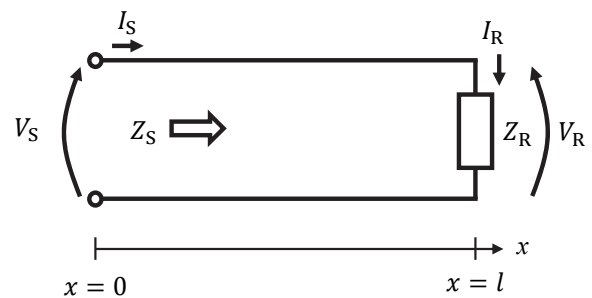


Fig. 2

II. Answer the following questions regarding a circuit with an N-type MOS transistor.

A voltage between the gate and source of the transistor is V_{GS} . The transistor has a threshold voltage V_{TH} , a drain current I_D , and a transconductance g_m . For several values of V_{GS} , DC drain voltage – drain current characteristics are shown in Fig. 3. The drain voltage at the inflection point is $V_{GS} - V_{TH}$ and the drain current at the point is proportional to $(V_{GS} - V_{TH})^2$. A small-signal equivalent circuit of the transistor is represented by Fig. 4.

(1) Express g_m by using V_{GS} , I_D , and V_{TH} when the transistor operates in the saturation region.

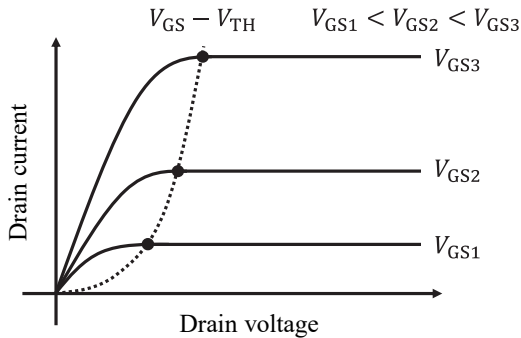


Fig. 3

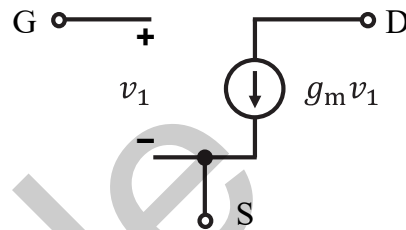


Fig. 4

A voltage-amplifier circuit that consists of a transistor M, resistors, and capacitors as shown in Fig. 5. The supply voltage is V_{DD} . Small-signal input and output voltages are v_{in} and v_{out} , and their Laplace transforms are $V_{in}(s)$ and $V_{out}(s)$, respectively. Here, s is a variable of the Laplace transform.

- (2) A drain current I_D flows through M when the supply voltage V_{DD} is applied. Then, find the maximum value of R_L when M operates in the saturation region, by using V_{DD} , V_{TH} , and I_D .
- (3) When M operates in the saturation region, draw a small-signal equivalent circuit of the circuit in Fig. 5.
- (4) When M operates in the saturation region, find a transfer function $\frac{V_{out}(s)}{V_{in}(s)}$.
- (5) Draw a Bode diagram of the transfer function in Question (4) with respect to the amplitude and the phase. Here, $C_1 R$ is sufficiently larger than $C_2 R_L$.
- (6) Find the angular frequency where the amplitude of the transfer function in Question (4) becomes unity at sufficiently high frequency.


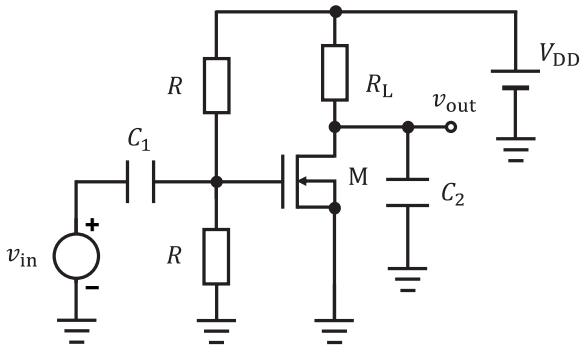


Fig. 5

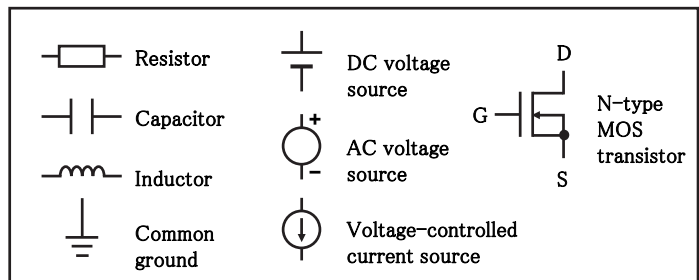

Legend