

## Problem 2

I. Answer the following questions on electric circuits. Here,  $s$  is a variable of the Laplace transform. Assume that  $L_1 > M$  and  $L_2 > M$  hold among the self inductances  $L_1$  and  $L_2$ , and the mutual inductance  $M$ . Symbols in the figures are defined in the legend.

- (1) As shown in Fig. 1, the currents  $I_1(s)$  and  $I_2(s)$  flow in two inductors with the self inductances  $L_1$  and  $L_2$ , respectively, and with the mutual inductance  $M$ . Find the self inductances  $L_\alpha$ ,  $L_\beta$ , and  $L_\gamma$  of the circuit in Fig. 2 that is equivalent to that in Fig. 1, using  $L_1$ ,  $L_2$ , and  $M$ .
- (2) In the AC bridge circuit shown in Fig. 3 with the angular frequency  $\omega$ , no current flows through the AC detector D. Find the self inductance  $L_2$  and the mutual inductance  $M$ . You may use the resistances  $R_A$ ,  $R_B$ ,  $R_C$ , the self inductance  $L_1$ , the capacitance  $C$ , and the angular frequency  $\omega$ , if necessary.

The circuit in Fig. 4 contains the DC voltage source  $E$ , the two identical resistors  $R$ , and the capacitor  $C$ . Assume that  $L_1 = L_2 = \sqrt{2}M$  holds in the following questions. The switch S had been opened for a sufficiently long time and then was closed at time  $t = 0$ . Damped oscillations are observed at  $t > 0$  in the currents flowing in the circuit.

- (3) Write the simultaneous equations that the currents  $I_1(s)$ ,  $I_2(s)$ , and  $I_3(s)$  satisfy at  $t > 0$ .
- (4) Find  $I_3(s)$ . It is not required to transform it to a time-domain form.
- (5) Find the range of capacitance  $C$  for generating the damped oscillation.

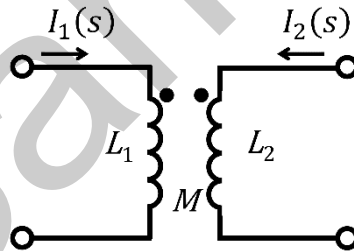
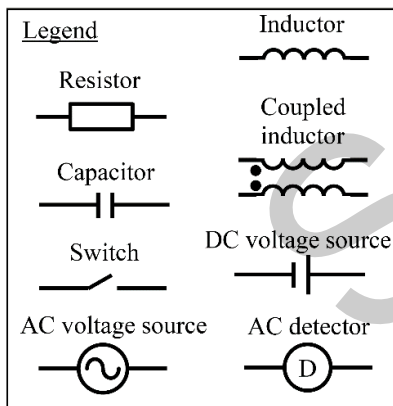


Fig. 1

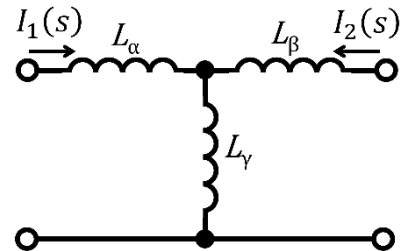


Fig. 2

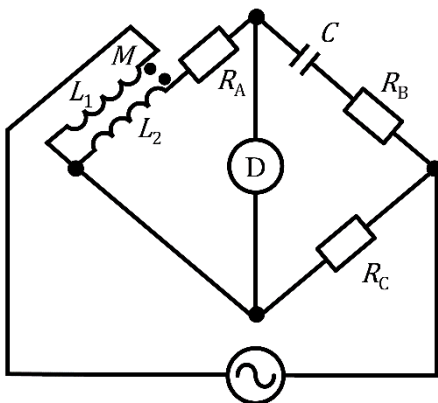


Fig. 3

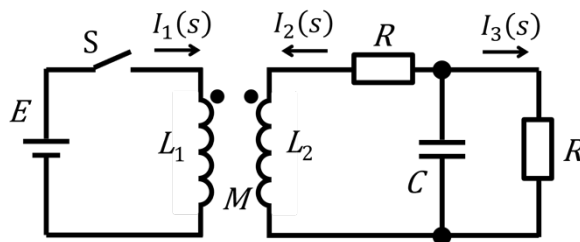


Fig. 4

II. Answer the following questions on circuits using N-type MOS transistors. The symbols in the figures are defined in the legend. Use the circuit in Fig. 5 as a small-signal equivalent circuit for an N-type MOS transistor. Here,  $g_m$  and  $v_{GS}$  are the transconductance and the gate-to-source voltage, respectively.

- (1) Draw a small-signal equivalent circuit for the circuit in Fig. 6.
- (2) The circuit in Fig. 6 receives a small-signal AC input  $v_{in}$ , which is a complex voltage with angular frequency  $\omega$ . Find the complex output voltage  $v_{out}$ .
- (3) Choose out of the following A and B a correct description regarding the characteristics of the circuit in Fig. 6. Briefly explain this reason. In addition, find the cutoff angular frequency of the circuit.
  - A. The circuit works as a low-pass filter.
  - B. The circuit works as a high-pass filter.

The circuit in Fig. 7 consists of the three circuits in Fig. 6. Oscillatory voltages occurred in this circuit. Here, the voltages in this circuit can be regarded as small signals.

- (4) Find the angular frequency of the oscillation.
- (5) Write the relation that the resistance  $R_L$  and the transconductance  $g_m$  satisfy for generating the oscillatory voltage.

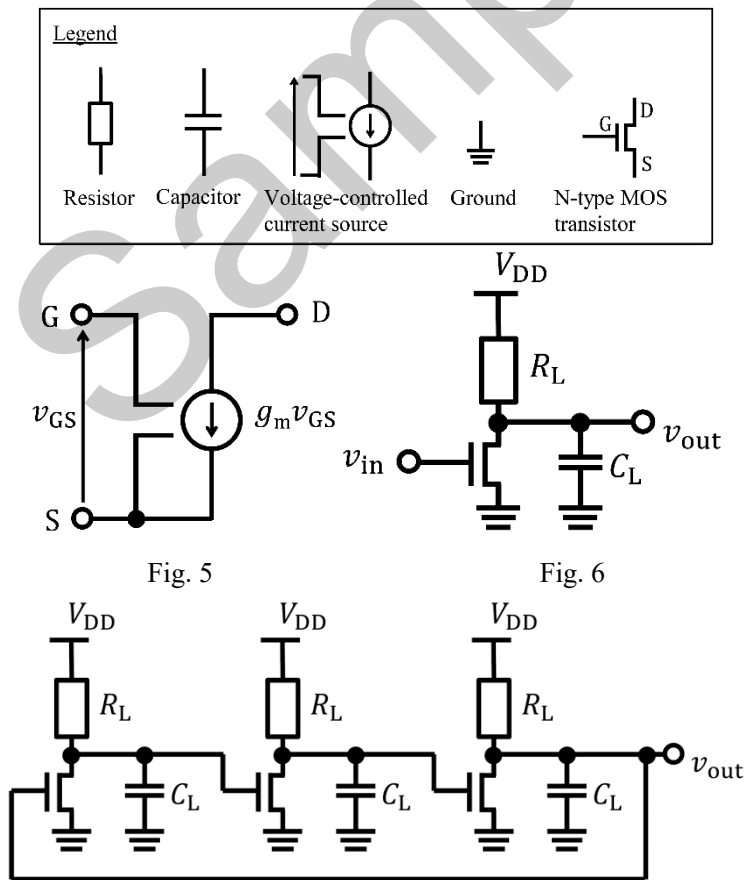


Fig. 7